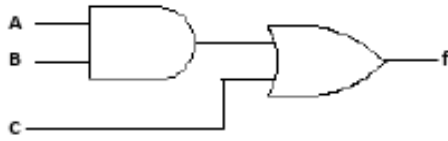




4.




Logic Equation

f = \_\_\_\_\_

Instructor's Initials: \_\_\_\_\_

TRUTH TABLE			
INPUT			OUTPUT
A	B	C	f

5.

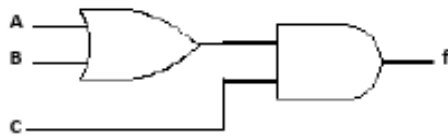


Logic Equation

f = \_\_\_\_\_

Instructor's Initials: \_\_\_\_\_

TRUTH TABLE			
INPUT			OUTPUT
A	B	C	f

6.

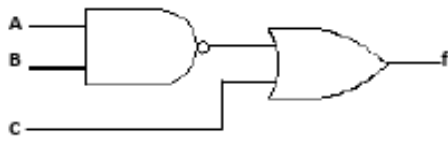


Logic Equation

f = \_\_\_\_\_

Instructor's Initials: \_\_\_\_\_

TRUTH TABLE			
INPUT			OUTPUT
A	B	C	f

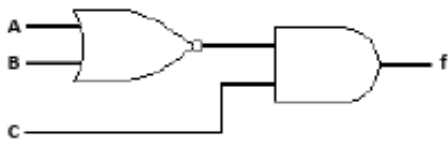

Logic Equation

f = \_\_\_\_\_

Instructor's Initials: \_\_\_\_\_

TRUTH TABLE			
INPUT			OUTPUT
A	B	C	f